

Name:

Enrolment No:



MANIPAL UNIVERSITY
JAIPUR

Odd Semester Mid Term Examination, Oct 2023

Faculty of Engineering| School of Computer and Communication Engineering

Department of IoT and IS

B. TECH – CSE (IoT & IS)

Course Code: IS2101 Course: Digital Design and Computer Architecture

Time: 1.5 hrs. Max. Marks: 30

Instructions: All questions are compulsory.

Missing data, if any, may be assumed suitably.

Calculator is not allowed.

SECTION A

S.No.

Write down “two address code” using register for the following equation:

$X=A+B/C$

Solution:

Q A1

LOAD B, R0

DIV C, R0

ADD A, R0

STORE R0, X

Suppose a system is 32-bit and memory is byte-addressable. Memory address begin with 1000. If the location has the value in (FF00AA11). Find and big-endian.

Solution:

FF00AA11

Big Endian: AA

Q A2

1000 1001 1002 1003

FF 00 AA 11

Little Endian: 00

1000 1001 1002 1003

11 AA 00 FF

What are universal gates and why they are called as universal gates.


Q A3

A universal gate is a gate which can implement any Boolean function without need to use any other gate type. The NAND and NOR gates are universal. NOR gates are economical and easier to fabricate and are the basic gates used in all IC digital logic families.

SECTION B

Design a 3 X 8 Decoder using two 2 X 4 Decoders.

Q B1

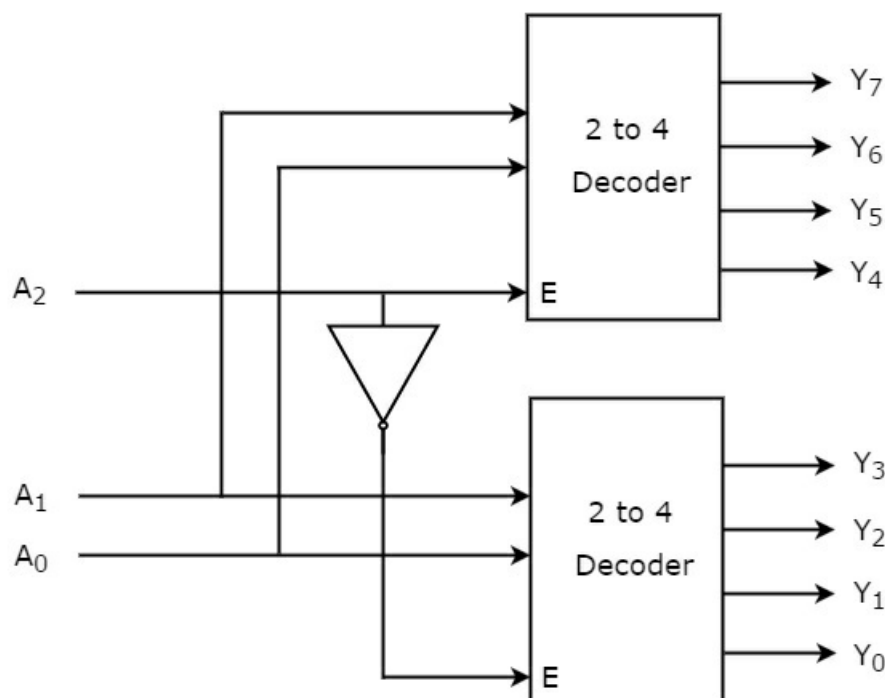

Q B2

Perform addition using 7-bit signed, 2's complement binary number representation, on the following pairs of decimal numbers. State whether overflow

1. $(-32)_{10}$ and $(-32)_{10}$
2. $(32)_{10}$ and $(32)_{10}$

Solution:

1 1 0 0 0 0 0 -32
1 1 0 0 0 0 0 -32
1 0 0 0 0 0 0 -64

Overflow= NO

0 1 0 0 0 0 0 32
0 1 0 0 0 0 0 32
1 0 0 0 0 0 0 +64

Overflow= YES

“Out of Range answer is arithmetically incorrect .


Identify the addressing mode in the following assembly instructions:

Q B3

- | | |
|--------------------|--------------------|
| 1. LOAD 20(R1), R5 | 1. MOVE R1, R2 |
| 2. MOVE #3000, R6 | 2. BRANCH > 0 LOOP |
| 3. ADD A, B | 3. ADD (R1), R2 |
| 4. CLEAR R0 | 4. ADD A, R0 |
-
1. LOAD 20(R1), R5: Indexed Mode
 2. MOVE #3000, R6: Immediate Mode
 3. ADD A, B: Absolute/Direct Mode
 4. CLEAR R0: Register Mode
 5. MOVE R1, R2: Register Mode
 6. BRANCH > 0 LOOP: Direct Mode
 7. ADD (R1), R2: Indirect Mode
 8. ADD A, R0: Direct and Register Mode Both

The shift register shown below is initially loaded with 1010. If the clock is applied continuously then after how many clocks pulses, the content of the

Q B4

 

Solution

Solution: 7 clock pulses

CLK	Q3	Q2	Q1	Q0	Q1 XOR Q0	S1=Q2 XOR Q1
X	1	0	1	0	1	
1	1	1	0	1	1	0
2	0	1	1	0	1	0
3	0	0	1	1	0	0
4	0	0	0	1	1	1
5	1	0	0	0	0	0
6	0	1	0	0	0	1
7	1	0	1	0		

SECTION-C

- A K-map with of three variable is shown below:

A \ BC	00	01	11	10
0	1		1	1
1	1	1		1

- Write the function for above mentioned k-map in the form of Sum of Min-terms.
- Write simplified function.

3. Draw the Logic Diagram.
4. Identify gate delay for the same.


Solution:

- Write the function for above mentioned k-map in the form of Sum of Min-terms

$$A'B'C' + AB'C' + AB'C + A'BC + A'BC' + ABC'$$

- Write simplified function.

$$C' + A \text{ xor } B$$

 

- Draw the Logic Diagram.
- Identify gate delay for the same.

Total Gate Delay: 2

Q C1